

Consider the following problem.

A system used 3 switches A, B and C; a combination of switches determines whether an alarm, X, sounds:

If switch A or switch B are in the ON position and if switch C is in the OFF position then a signal to sound an alarm, X is produced.

It is possible to convert this problem into a logic statement.

So we get:

If  $(A = 1 \text{ OR } B = 1)$       **AND**       $(C = \text{NOT } 1)$       then  $X = 1$


↑  
The first part is two inputs (A and B) joined by an OR gate

↑  
The output from the first part and the third part are joined by an AND gate

↑  
The third part is one input (C) which is put through a NOT gate

Remembering that ON = 1 and OFF = 0; also remember that we write 0 as NOT 1.

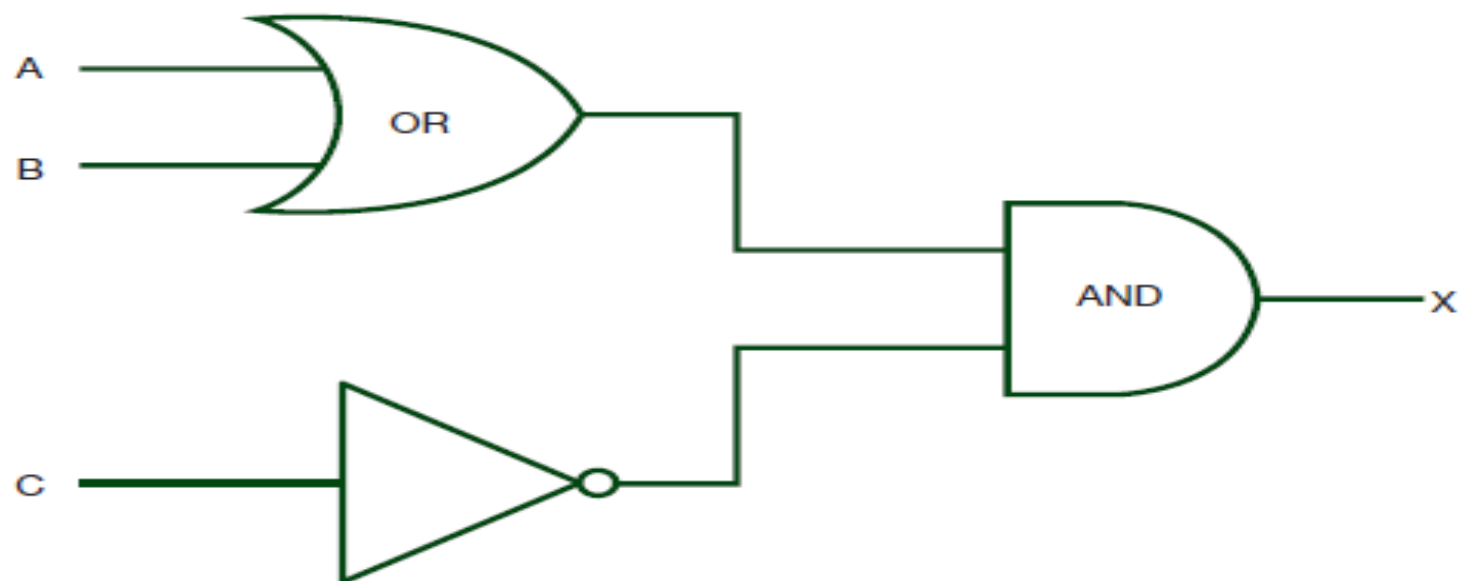So we get the following logic circuit (network):



This gives the following truth table:

INPUT A	INPUT B	INPUT C	OUTPUT X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

⦿ A traffic light system uses logic gates as part of the control system. The system is operated when the output D has the value 1. This happens when:

either (a) signal A is red

or (b) signal A is green and signals B and C are both red

(NOTE: You may assume for this problem that red = 0 and green = 1).

Design a logic circuit (network) and draw the truth table for the above system.

- ⦿ A chemical process gives out a warning signal ( $W = 1$ ) when the process operates incorrectly. A logic circuit (network) is used to monitor the process and to determine whether  $W = 1$ .

Inputs	Binary values	Description of plant status
C	1	Chemical rate = 20 litres/second
	0	Chemical rate < 20 litres/second
T	1	Temperature = 91°C
	0	Temperature > 91°C
X	1	Concentration > 5M
	0	Concentration = 5M

A warning signal ( $W = 1$ ) will be generated if:  
either (a) Chemical rate  $< 20$  litres/second  
or (b) Temperature  $> 91^{\circ}\text{C}$  and Concentration  $> 5\text{M}$   
or (c) Chemical rate  $= 20$  litres/second and  
Temperature  $> 91^{\circ}\text{C}$

Draw a logic circuit (network) and truth table to  
show all the  
possible situations when the warning signal could be  
received.

- A nuclear power station has a safety system based on three inputs to a logic circuit (network). A warning signal ( $S = 1$ ) is produced when certain conditions in the nuclear power station occur based on these three inputs.

Inputs	Binary values	Description of plant status
T	1	Temperature > 115°C
	0	Temperature ≤ 115°C
P	1	Reactor pressure > 15 bar
	0	Reactor pressure ≤ 15 bar
W	1	Cooling water > 120 litres/hour
	0	Cooling water ≤ 120 litres/ hour

A warning signal ( $S = 1$ ) will be produced when any of the following occurs:

either (a) Temperature  $> 115$  C and Cooling water  $\leq 120$  liters/hour

or (b) Temperature  $\leq 115$  C and Reactor pressure  $> 15$  bar or Cooling water  $\leq 120$  liters/hour

Draw a logic circuit (network) and truth table to show all the possible situations when the warning signal ( $S$ ) could be received.